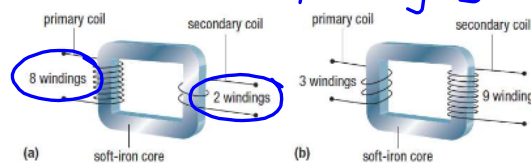


SPH3U 13.5 Transformers**1. How transformers work**

Transformer:	a device that can raise or lower voltage.
AC	transformers <u>only</u> work in AC!
how it works	like a Faraday's Ring. a coil of wire on the left induces current in a coil on the right. the AC means a constantly changing magnetic field!



$$P_p = P_s$$

$$V_p I_p = V_s I_s$$

Step-down transformer:	reduces voltage (increases current). primary windings > secondary windings
Step-up transformer:	increases voltage (reduces current). primary windings < secondary windings.
Conservation of energy:	$\therefore P_p = P_s \quad \therefore P = VI, V_p I_p = V_s I_s.$
Equations:	$\frac{V_p}{V_s} = \frac{N_p}{N_s}, \quad \frac{I_s}{I_p} = \frac{N_p}{N_s}, \quad \frac{I_s}{I_p} = \frac{V_p}{V_s}.$

$N = \#$ of windings.

A step-down transformer used in an adapter for a laptop has a primary voltage of 120 V. There are 250 windings in the primary coil and 25 windings in the secondary coil. Calculate the voltage in the secondary coil.

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} \rightarrow V_p = V_s \times \frac{N_p}{N_s} \rightarrow V_s = V_p \times \frac{N_s}{N_p} = 120 \times \frac{25}{250} = \underline{\underline{12V}}.$$

A step-down transformer used in the adapter for a cellphone charger has a primary voltage of 120 V and a secondary voltage of 5.0 V. The current in the primary coil is 0.10 A. Calculate the current in the secondary coil.

$$\frac{I_s}{I_p} = \frac{V_p}{V_s} \rightarrow I_s = I_p \times \frac{V_p}{V_s} = 0.1 \times \frac{120}{5} = \underline{\underline{2.4A}}.$$

Homework: page 609: #2, 7-9