

SPH3U 11.8 Resistors in Circuits

1. Series and parallel


Equivalent resistance:	the total resistance of a group of resistors.
Series:	$I_S R_S = I_1 R_1 + I_2 R_2 + I_3 R_3 \quad (I_1 = I_2 = \dots = I_S)$ $V_{\text{series}} = V_1 + V_2 + V_3 \rightarrow I_S R_S = I_S (R_1 + R_2 + R_3).$
equation	$R_{\text{series}} = R_1 + R_2 + R_3 + \dots$

Four resistors are connected in series in a circuit. The resistances are as follows: $R_1 = 41 \Omega$, $R_2 = 51.75 \Omega$, $R_3 = 11.1 \Omega$, $R_4 = 102.008 \Omega$. Calculate the equivalent resistance.

$$\begin{aligned}
 R_S &= R_1 + R_2 + R_3 + R_4 \\
 &= 41 + 51.75 + 11.1 + 102.008 \\
 &= \underline{\underline{206 \Omega}}.
 \end{aligned}$$

$V = IR$ $I = \frac{V}{R}$	Parallel:	$I_P = I_1 + I_2 + I_3 \rightarrow \frac{V_P}{R_P} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \quad (V_1 = V_2 = V_3 = V_P).$ $\frac{V_P}{R_P} = V_P \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$
equation		$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \rightarrow R_P = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$

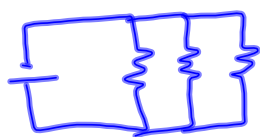Three resistors are connected in parallel in a circuit. The resistances are as follows: $R_1 = 15 \Omega$, $R_2 = 12 \Omega$, $R_3 = 10 \Omega$. Calculate the equivalent resistance.



$$\begin{aligned}
 \frac{1}{R_P} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\
 &= \frac{1}{15} + \frac{1}{12} + \frac{1}{10} \\
 &= \frac{4}{60} + \frac{5}{60} + \frac{6}{60} \\
 &= \frac{15}{60} = \underline{\underline{\frac{1}{4}}}.
 \end{aligned}$$

$$\therefore R_P = \underline{\underline{4 \Omega}}.$$


2. Mixed circuits

Calculate the equivalent resistance for the circuit shown.

$$\begin{aligned}\frac{1}{R_p} &= \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \\ &= \frac{1}{75} + \frac{1}{50} + \frac{1}{30} \\ &= 0.067\end{aligned}$$

$$R_p = \underline{\underline{15\Omega}}$$
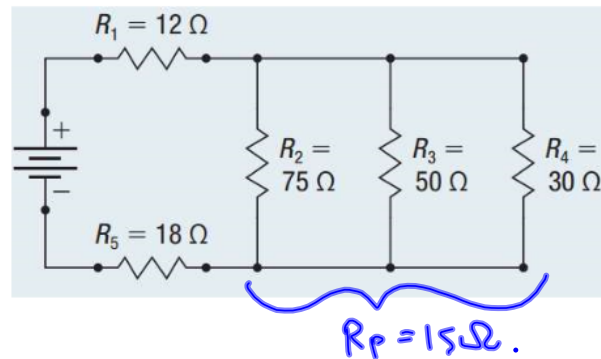
$$\begin{aligned}R_T &= R_1 + R_p + R_5 \\ &= 12 + 15 + 18 \\ &= \underline{\underline{45\Omega}}\end{aligned}$$



Homework: page 530: #4-5